



Abdullah Gül University

Department of Electrical and Electronics
Engineering

Pre-Lab 4

RLC Circuit Phasor Analysis

Barış DEMİRCİ agu@338.rocks

December 25, 2024

Contents

1	Overview	3
1.1	Objective	3
2	Procedure	4
2.1	Analytical Calculations in Phasor Domain	4
2.1.1	Determine the Capacitor Value	4
2.1.2	Calculating Voltage and Current Values	5
2.2	SPICE Simulation	7
3	Discussion	8
3.1	Analytical Results	8
3.2	Simulation Analysis	8
4	Conclusion	9

Chapter 1

Overview

1.1 Objective

This pre-lab report focuses on analyzing and simulating an RLC circuit, as shown in Figure 1. The circuit is described by the equation $V_R + V_L = 2 \cos(\omega t - 7.5)$ with a frequency of $f = 1\text{kHz}$, $\omega = 2\pi \times 10^3 \frac{\text{rad}}{\text{s}}$. The objectives include calculating the capacitor value C and determining the phasor-domain voltage and current values (V_C , I_i , and I_o). Additionally, the circuit will be simulated in LTspice to observe the waveforms for voltages V_C and V_L , as well as currents I_i and I_o .

Chapter 2

Procedure

2.1 Analytical Calculations in Phasor Domain

2.1.1 Determine the Capacitor Value

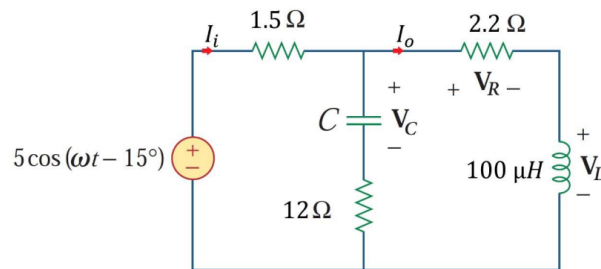


Figure 2.1: RLC Circuit

Transforming this circuit into the phasor domain, we have the following circuit:

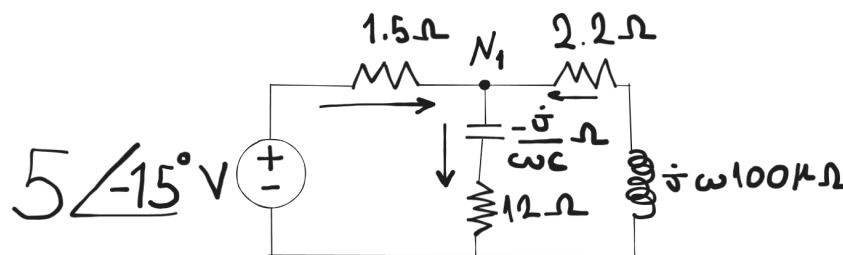


Figure 2.2: RLC Circuit Phasor Domain

Applying nodal analysis at node N_1 :

$$\frac{V_S - N_1}{1.5} + \frac{N_1}{2.2 + j2\pi \times 10^{-1}} - \frac{N_1}{12 + \frac{-j}{2000\pi C}} = 0 \quad (2.1)$$

V_S and N_1 are given as $V_S = 5 \angle -15^\circ$ and $N_1 = 2 \angle -7.5^\circ$.

Solving for C :

$$\frac{5\angle-15^\circ - 2\angle-7.5^\circ}{1.5} + \frac{2\angle-7.5^\circ}{2.2 + j2\pi \times 10^{-1}} - \frac{2\angle-7.5^\circ}{12 + \frac{-j}{2000\pi C}} = 0 \quad (2.2)$$

$$\frac{5\angle-15^\circ - 2\angle-7.5^\circ}{1.5} + \frac{2\angle-7.5^\circ}{2.2 + j2\pi \times 10^{-1}} = \frac{2\angle-7.5^\circ}{12 + \frac{-j}{2000\pi C}} \quad (2.3)$$

$$2.0189\angle-19.9451^\circ + 0.8741\angle-23.4393^\circ = \frac{2\angle-7.5^\circ}{12 + \frac{-j}{2000\pi C}} \quad (2.4)$$

$$2.8919\angle-21.0007^\circ = \frac{2\angle-7.5^\circ}{12 + \frac{-j}{2000\pi C}} \quad (2.5)$$

$$\frac{-j}{2000\pi C} = \frac{2\angle-7.5^\circ}{2.8919\angle-21.0007^\circ} - 12 = 11.3287\angle179.1834^\circ \quad (2.6)$$

$$C = \frac{-j}{2000\pi \times 11.3287\angle179.1834^\circ} = 1.4049\angle90.8166^\circ = -200.2236 \times 10^{-9} + j14.0474 \times 10^{-6} \quad (2.7)$$

From equation 2.7, we have $C = -200.2236 \times 10^{-9} + j14.0474 \times 10^{-6}$, which means there should be a capacitor with a real value which is impossible. Therefore, we can add a $200.2236 \times 10^{-9}\Omega$ resistor in series to the capacitor to make it only capacitive. After that, the capacitor value is $j14.0474\mu\Omega$.

2.1.2 Calculating Voltage and Current Values

After finding the capacitor value, we know everything about the circuit. We can calculate the Voltage and current values as follows:

$$I_O = \frac{2\angle-7.5^\circ}{2.2 + j2\pi \times 10^{-1}} = 0.802\angle-3.4771^\circ A \quad (2.8)$$

$$I_i = \frac{5\angle-15^\circ - 2\angle-7.5^\circ}{1.5} = 2.0189\angle-19.9451^\circ A \quad (2.9)$$

$$I_C = I_i - I_O = 1.2703\angle-30.255^\circ A \quad (2.10)$$

And from the current values, we can calculate the voltage values:

$$V_R = I_O \times 2.2 = 1.7644\angle-3.4771^\circ V \quad (2.11)$$

$$V_L = I_O \times j2\pi \times 10^{-1} = 0.50391\angle86.5229^\circ V \quad (2.12)$$

$$V_C = I_C \times j14.0474\mu = 1.7844\angle59.745^\circ V \quad (2.13)$$

Converting the phasor voltages and currents to time domain:

$$v_R(t) = 1.7644 \cos(2000\pi t - 3.4771^\circ) V \quad (2.14)$$

$$v_L(t) = 0.50391 \cos(2000\pi t + 86.5229^\circ) V \quad (2.15)$$

$$v_C(t) = 1.7844 \cos(2000\pi t + 59.745^\circ) V \quad (2.16)$$

$$i_O(t) = 0.802 \cos(2000\pi t - 3.4771^\circ) A \quad (2.17)$$

$$i_i(t) = 2.0189 \cos(2000\pi t - 19.9451^\circ) A \quad (2.18)$$

$$i_C(t) = 1.2703 \cos(2000\pi t - 30.255^\circ) A \quad (2.19)$$

2.2 SPICE Simulation

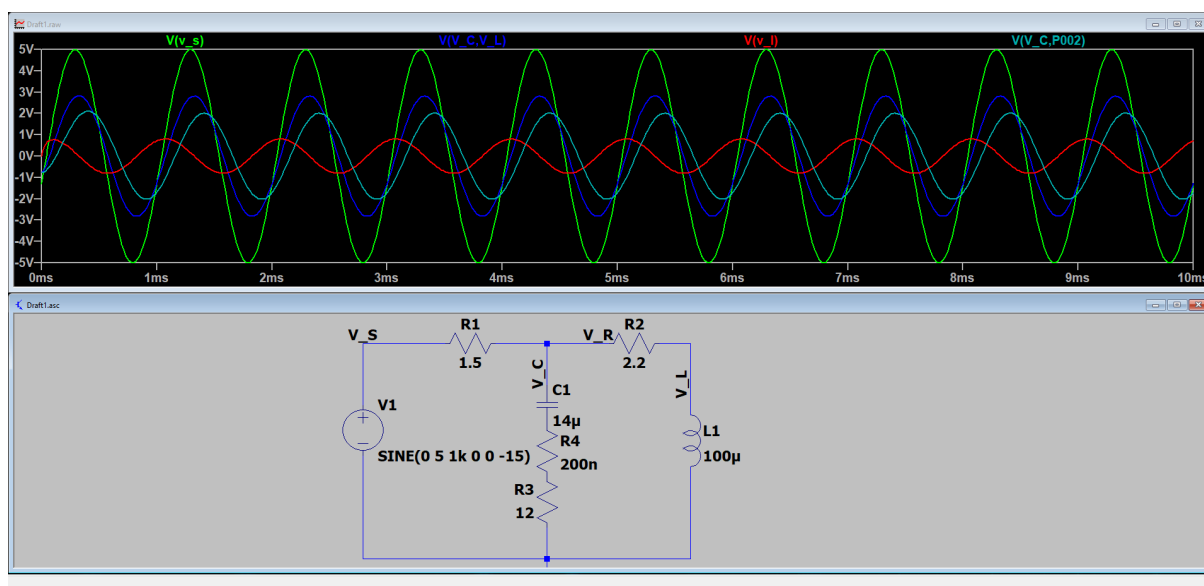


Figure 2.3: SPICE Voltage Simulation

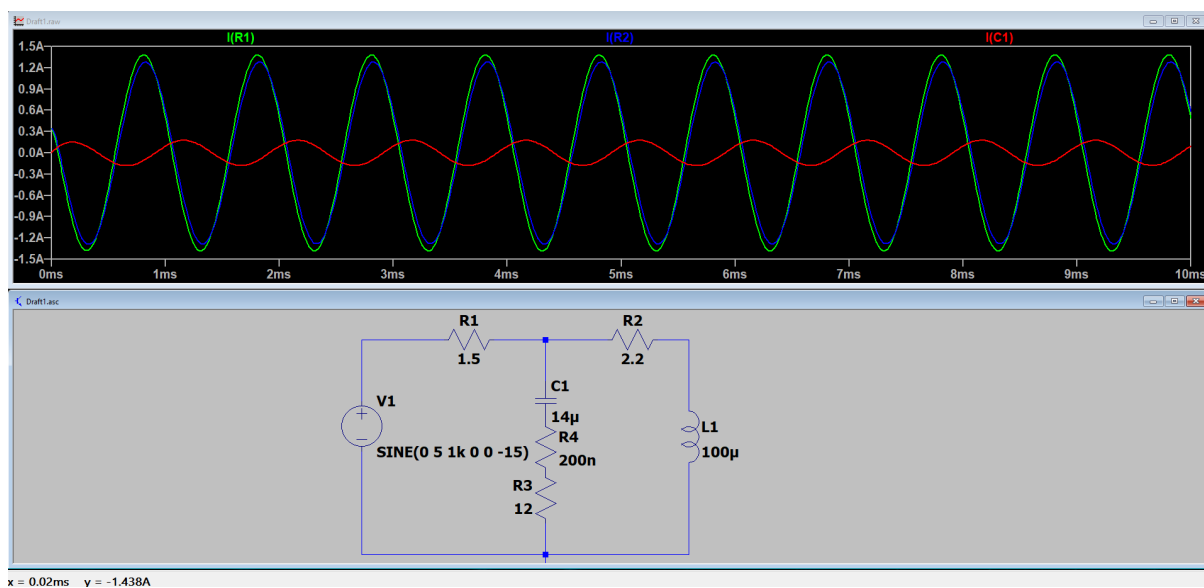


Figure 2.4: SPICE Current Simulation

Comparing the SPICE simulation results with the analytical calculations, everything seems to be correct.

Chapter 3

Discussion

3.1 Analytical Results

The calculated capacitor value, voltage, and currents are based on phasor-domain principles. These results highlight the phase differences and magnitude relationships inherent in RLC circuits operating at a specific frequency.

3.2 Simulation Analysis

The SPICE simulation provides a practical visualization of the circuit's behavior. Waveforms for and demonstrate the phase shifts due to the reactive components, while and reflect the current distribution through the circuit.

Chapter 4

Conclusion

This pre-lab exercise has provided a comprehensive approach to understanding RLC circuit dynamics. By combining phasor-domain analysis with SPICE simulations, we have:

- Determined the capacitor value required for circuit functionality.
- Calculated key voltage and current parameters.
- Visualized the circuit's behavior through simulation.

These steps ensure **readiness for the lab experiment** and a deeper understanding of the theoretical and practical considerations of RLC circuits.