



# **Abdullah Gül University**

Department of Electrical and Electronics  
Engineering

## **Pre-Lab 3**

Laplace Transform

Barış DEMİRCİ    agu@338.rocks

December 8, 2024

# Contents

<b>1</b>	<b>Overview</b>	<b>3</b>
1.1	Objective . . . . .	3
<b>2</b>	<b>Procedure</b>	<b>4</b>
2.1	RLC Circuit Analysis . . . . .	4
2.1.1	Transfer Function Derivation . . . . .	4
2.1.2	AC Sweep Analysis Simulation . . . . .	5
2.1.3	Transient Analysis Simulation . . . . .	7
2.1.4	Unit Step Response . . . . .	9
2.2	Op-Amp Circuit Analysis . . . . .	11
2.2.1	Transfer Function Derivation . . . . .	11
<b>3</b>	<b>Discussion</b>	<b>15</b>
<b>4</b>	<b>Conclusion</b>	<b>16</b>

# Chapter 1

## Overview

### 1.1 Objective

This pre-lab focuses on using the Laplace Transform to analyze circuits in the frequency domain. By applying these techniques, the transient and steady-state behavior of circuits can be fully understood. The experiment uses LTSpice to simulate and analyze RLC circuits and op-amp configurations in both the s-domain and time domain. These are the main objectives:

- To derive transfer functions from circuit elements.
- To validate analytical transfer functions through AC Sweep and transient simulations.
- To compare the performance of RLC circuits and op-amp designs using both analytical and simulated approaches.

# Chapter 2

## Procedure

### 2.1 RLC Circuit Analysis

#### 2.1.1 Transfer Function Derivation

In order to derive the voltage gain transfer function ( $H_V(s)$ ), we must first convert the circuit from time domain to the s-domain. The circuit is shown in Figure 2.1.

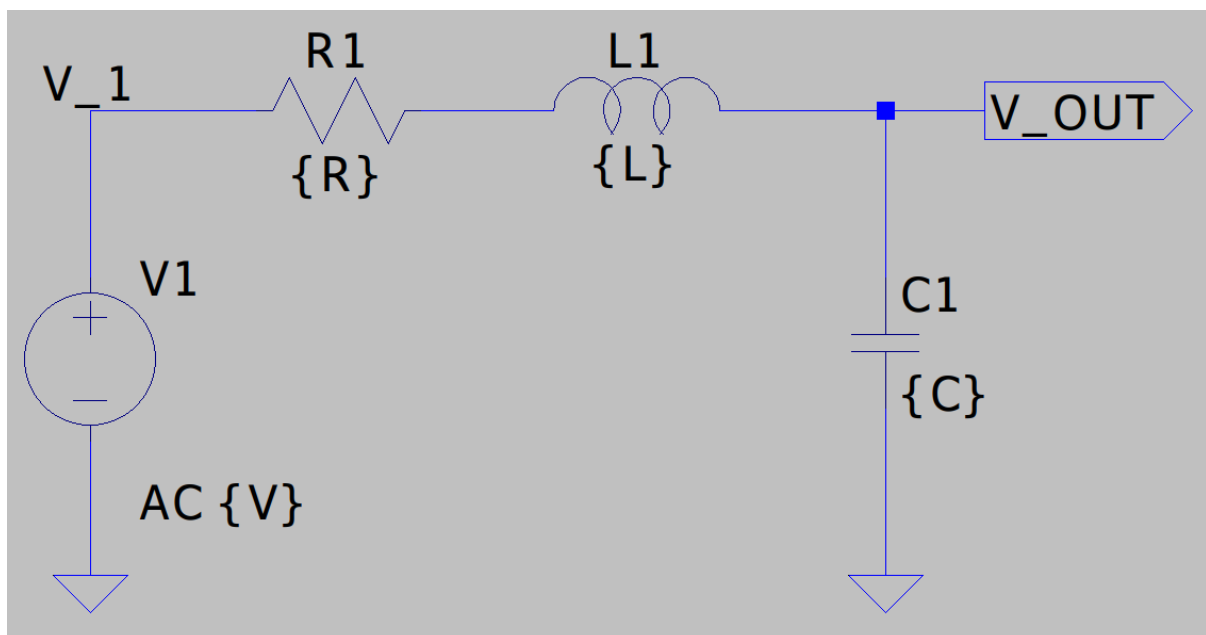


Figure 2.1: RLC Circuit

Where:

- $V_1$  is  $1V_{pp}$  input voltage.
- $V_{out}$  is the output voltage.
- $R$  is  $1k\Omega$  resistor.
- $L$  is  $1mH$  inductor.
- $C$  is  $0.1\mu F$  capacitor.

To find the transfer function, we first transform the circuit to the s-domain. The impedance of the resistor, inductor, and capacitor are given by:

$$\begin{aligned} Z_R &= R \\ Z_L &= sL \\ Z_C &= \frac{1}{sC} \end{aligned}$$

And the KVL equation for the circuit is:

$$\begin{aligned} V_1 &= V_R + V_L + V_C \\ V_1 &= IZ_R + IZ_L + IZ_C \\ V_1 &= I\left(R + sL + \frac{1}{sC}\right) \end{aligned}$$

Where  $I$  is the current through the circuit. The voltage gain transfer function is then:

$$\begin{aligned} H_V(s) &= \frac{V_{out}}{V_1} = \frac{I \frac{1}{sC}}{I\left(R + sL + \frac{1}{sC}\right)} \\ &= \frac{\frac{1}{sC}}{R + sL + \frac{1}{sC}} \end{aligned}$$

$$H_V(s) = \frac{1}{sRC + s^2LC + 1}$$

### 2.1.2 AC Sweep Analysis Simulation

To validate the transfer function, we will perform an AC Sweep analysis in LTSpice. The AC Sweep analysis will sweep the frequency of the input voltage from  $101Hz$  to  $120kHz$ . The output voltage will be measured and compared to the transfer function.

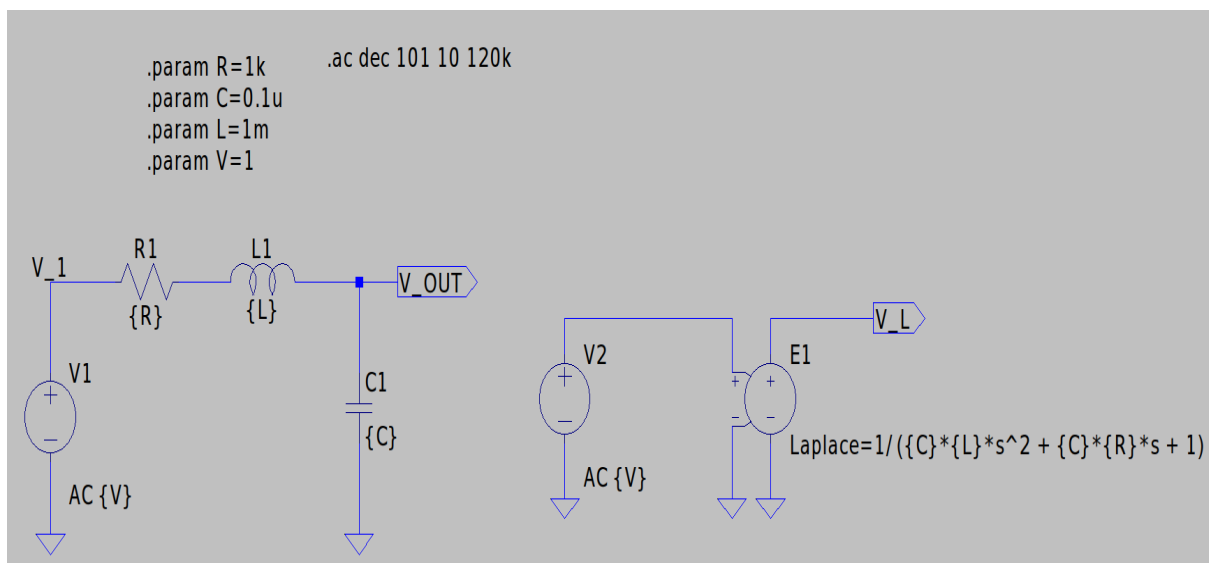
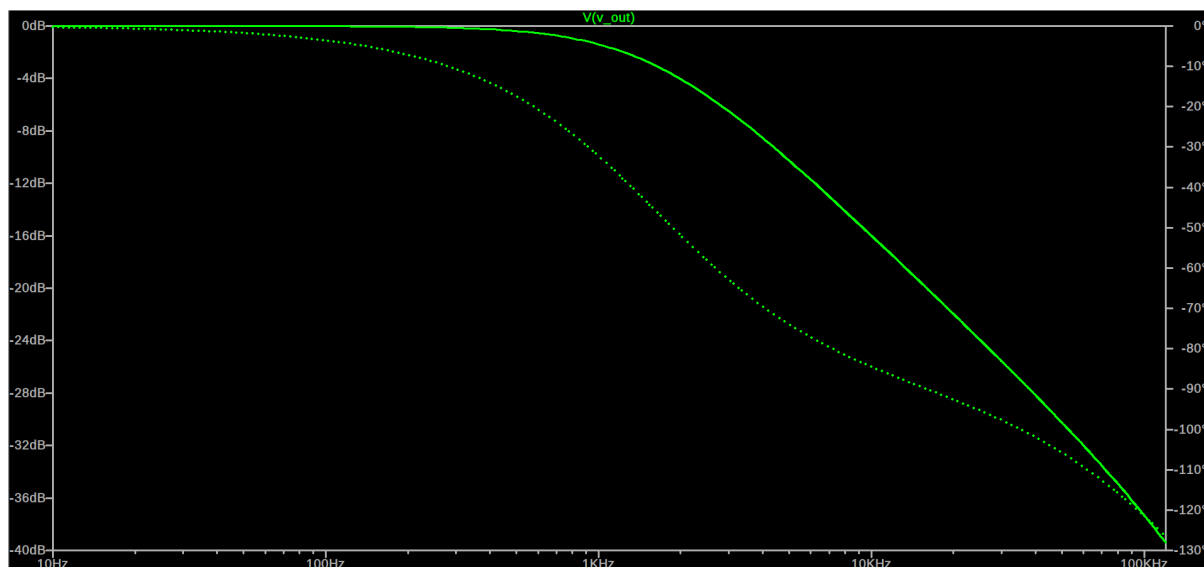
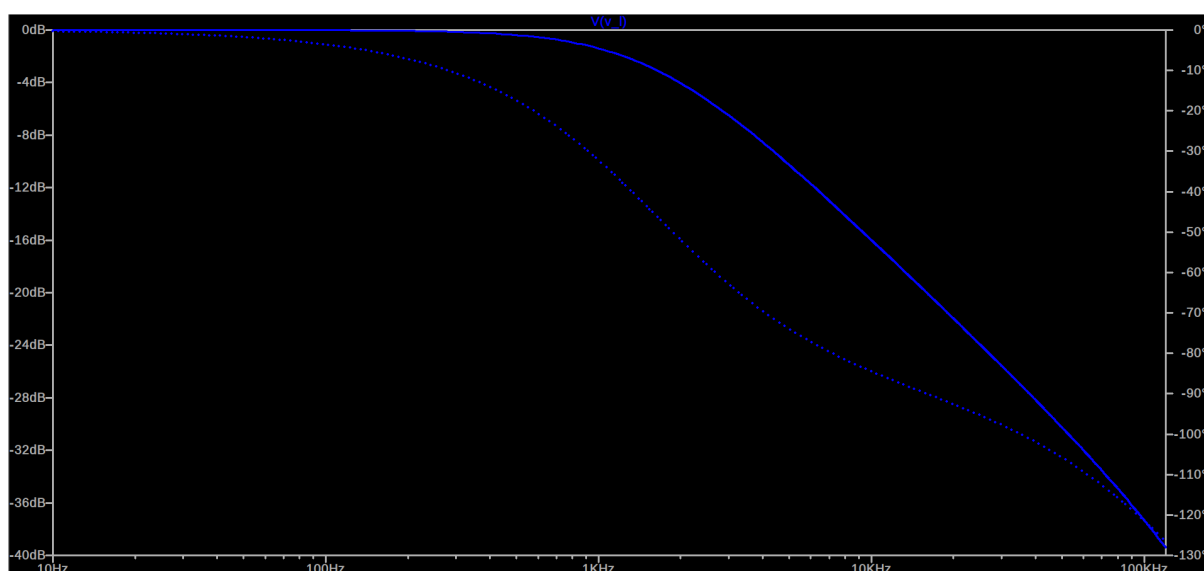


Figure 2.2: AC Sweep Analysis Simulation Setup

Figure 2.3:  $V_{out}$  Bode PlotFigure 2.4:  $H_V(s)$  Bode Plot

As shown in Figure 2.3, output voltage frequency response matches the transfer function  $H_V(s)$  as shown in Figure 2.4.

### 2.1.3 Transient Analysis Simulation

To further validate the transfer function, we will perform a transient analysis in LTSpice. Changed the input voltage  $V_{ac}$  to a  $1V_{pp}$  sine wave at  $10kHz$ . The output voltage will be measured and compared to the transfer function.


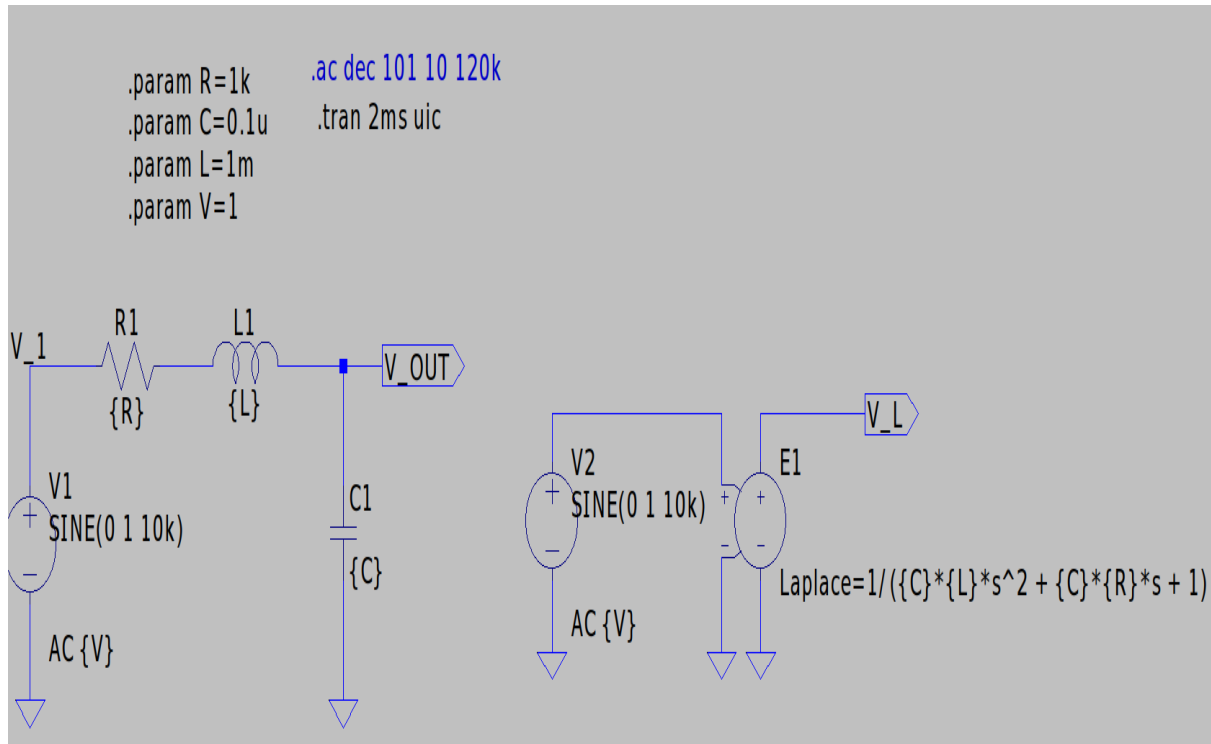
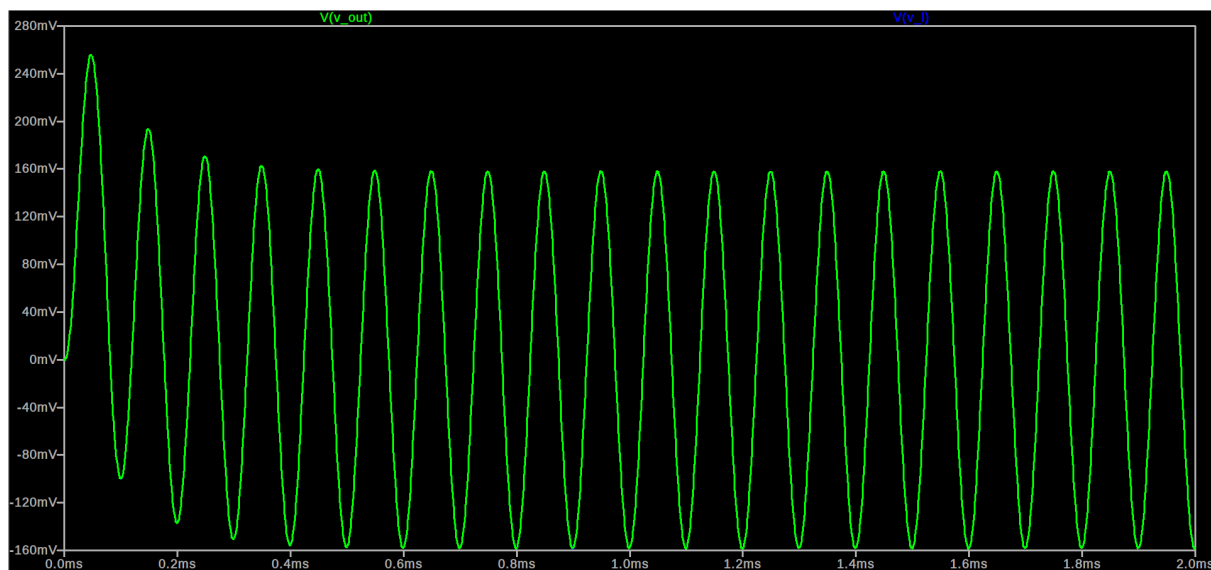


Figure 2.5: Transient Analysis Simulation Setup

Figure 2.6:  $V_{out}$  Transient ResponseFigure 2.7:  $H_V(s)$  Transient Response

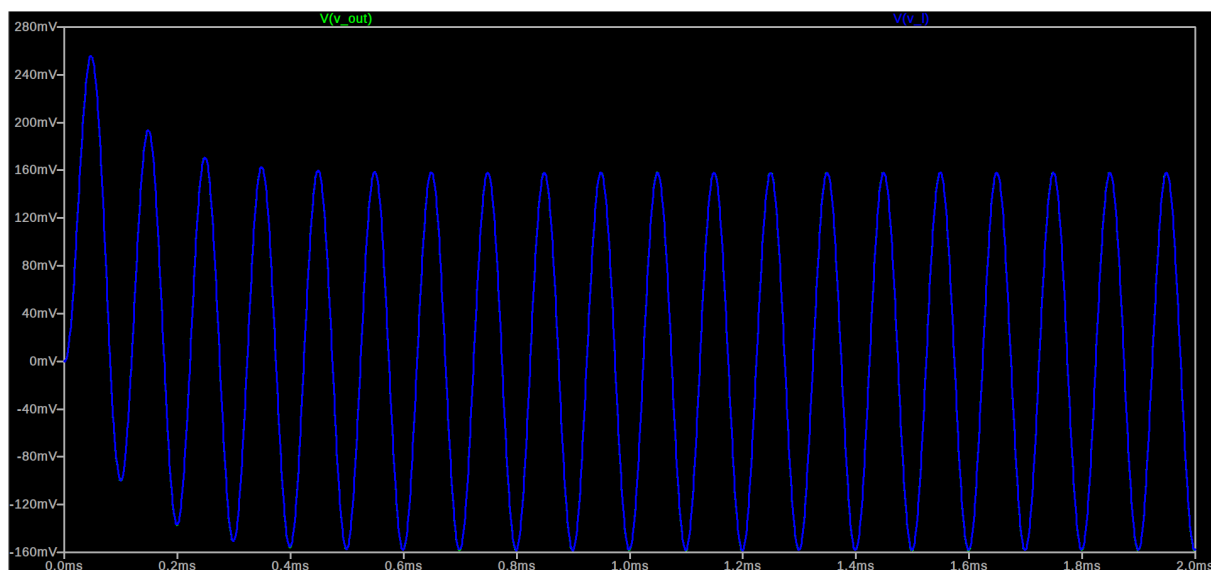As shown in Figure 2.6, output voltage matches the transfer function  $H_V(s)$  as shown in Figure 2.7.



### 2.1.4 Unit Step Response

Unit step response can show the transient behavior of the circuit. In order to find unit step response, Heaviside step function ( $u(t)$ ) is used as input voltage.

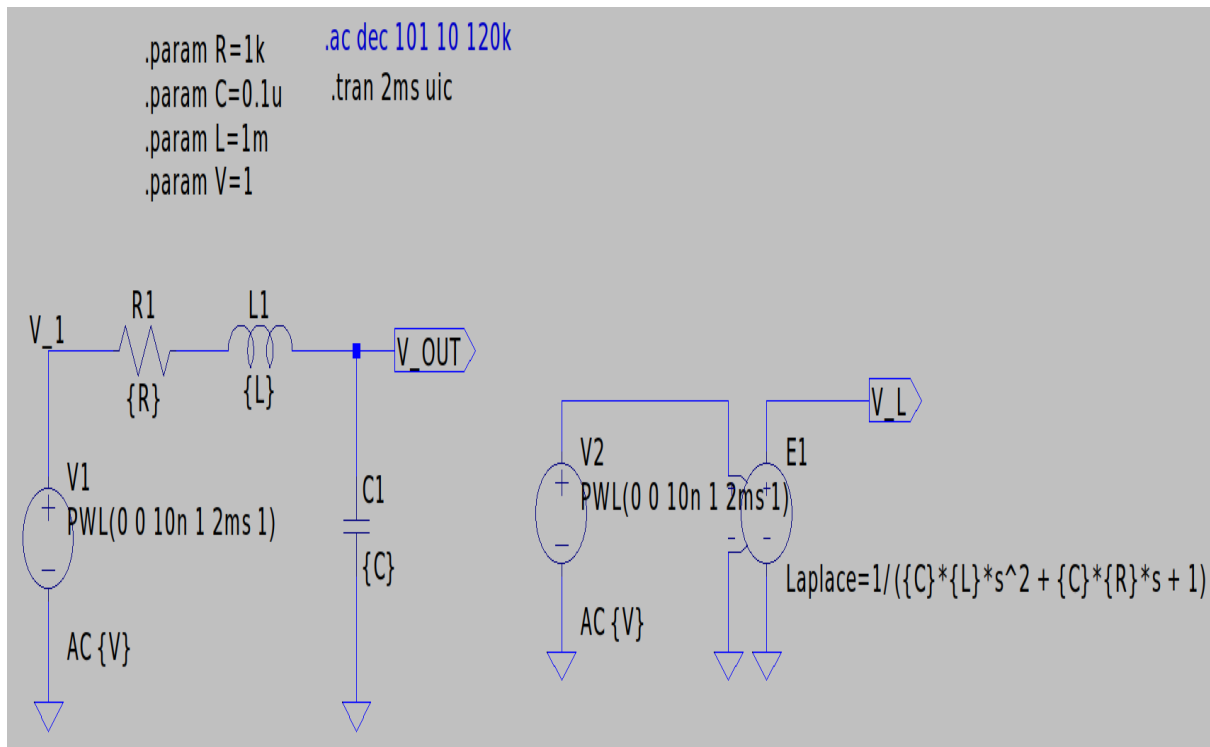
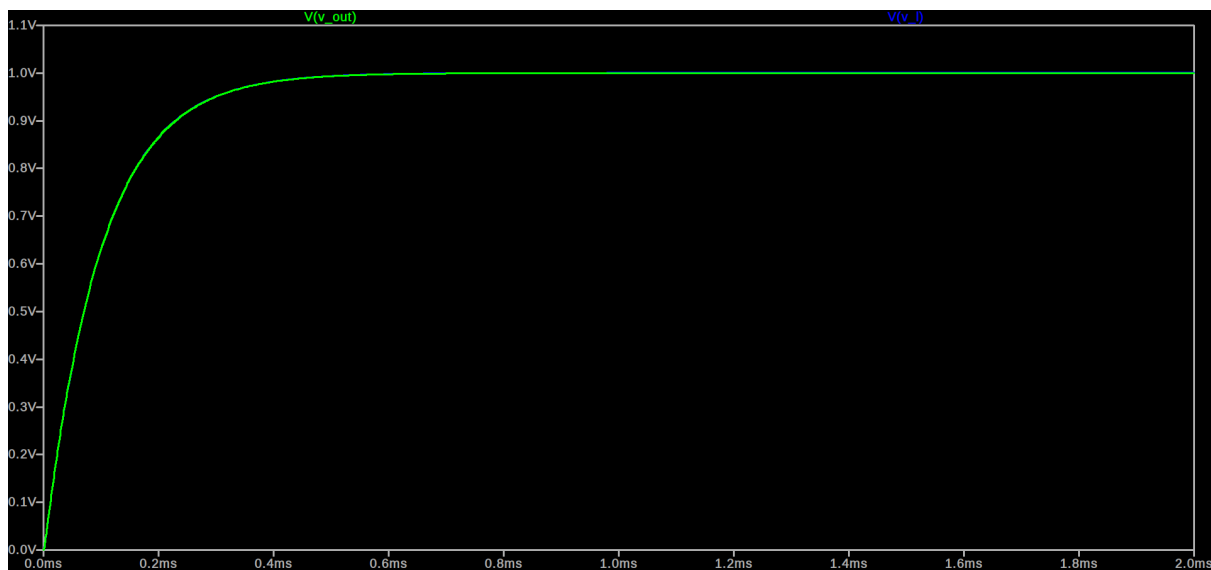
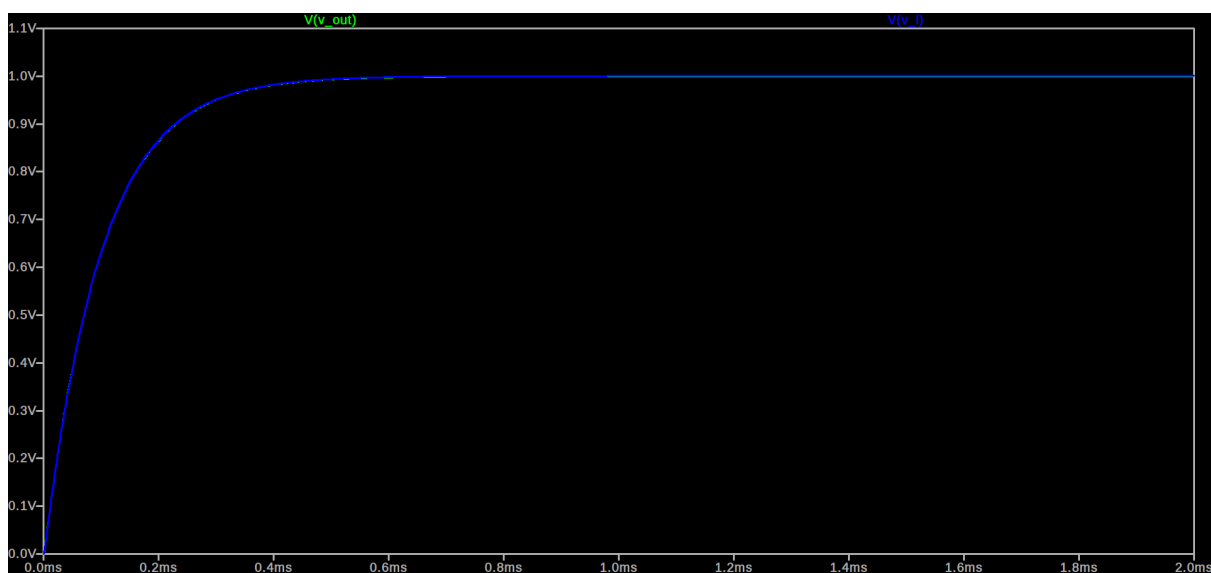


Figure 2.8: Unit Step Response Simulation Setup

Figure 2.9:  $V_{out}$  Unit Step ResponseFigure 2.10:  $H_V(s)$  Transient Response

As shown in Figure 2.9, output voltage matches the transfer function  $H_V(s)$  as shown in Figure 2.10.

## 2.2 Op-Amp Circuit Analysis

### 2.2.1 Transfer Function Derivation

In order to derive the voltage gain transfer function ( $H_V(s)$ ), we must first convert the circuit from time domain to the s-domain. The circuit is shown in Figure 2.11.

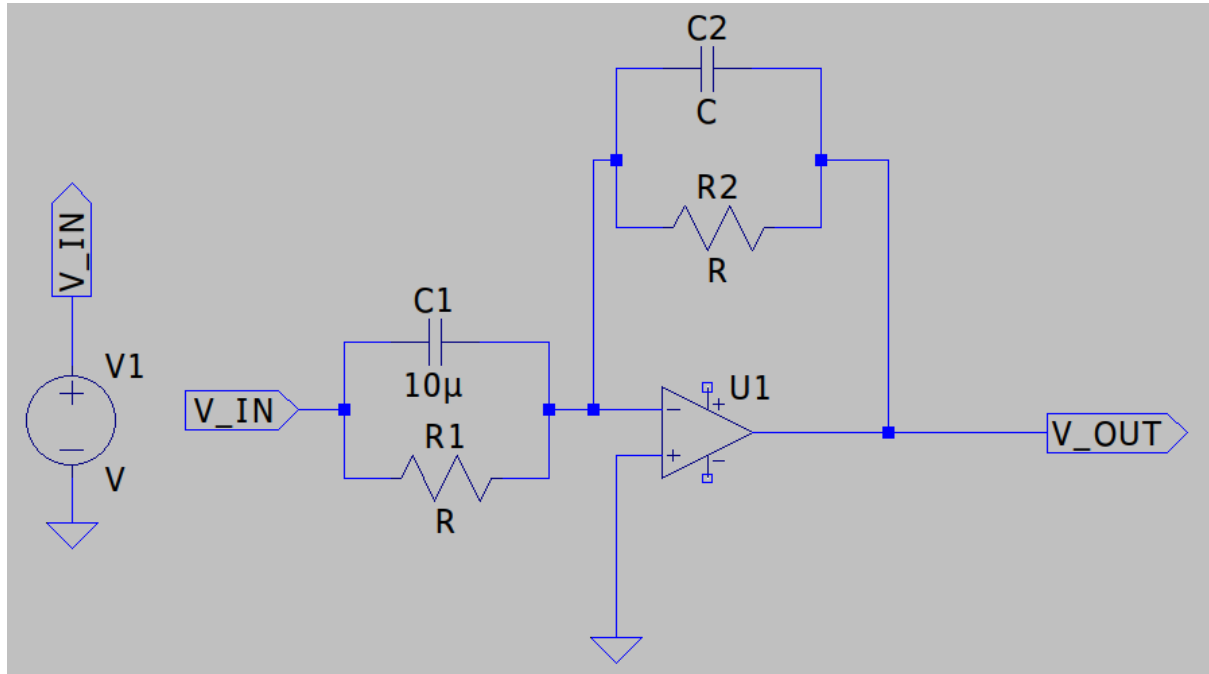


Figure 2.11: Op-Amp Circuit

Expected transfer function is  $H_V(s) = \frac{V_o}{V_i} = -\frac{s+1000}{2(s+4000)}$ :

$$\begin{aligned}
 \text{let } Z_1 &= \frac{R_1}{1 + C_1 R_1 s} \\
 \text{let } Z_2 &= \frac{R_2}{1 + C_2 R_2 s} \\
 \frac{V_{in}}{Z_1} &= -\frac{V_{out}}{Z_2} \\
 V_{out} &= -\frac{Z_2}{Z_1} V_{in} \\
 \Rightarrow H_V(s) &= -\frac{Z_2}{Z_1} = -\frac{s + 1000}{2(s + 4000)} \\
 \frac{s + 1000}{2(s + 4000)} &= \frac{C_1}{C_2} \cdot \left[ \frac{s + \frac{1}{R_1 C_1}}{s + \frac{1}{R_2 C_2}} \right] \\
 \Rightarrow C_1 &= 10\mu F, C_2 = 20\mu F, R_1 = 100\Omega, R_2 = 12.5\Omega
 \end{aligned}$$

Using these values, bode plot of the circuit and transfer function is shown below:

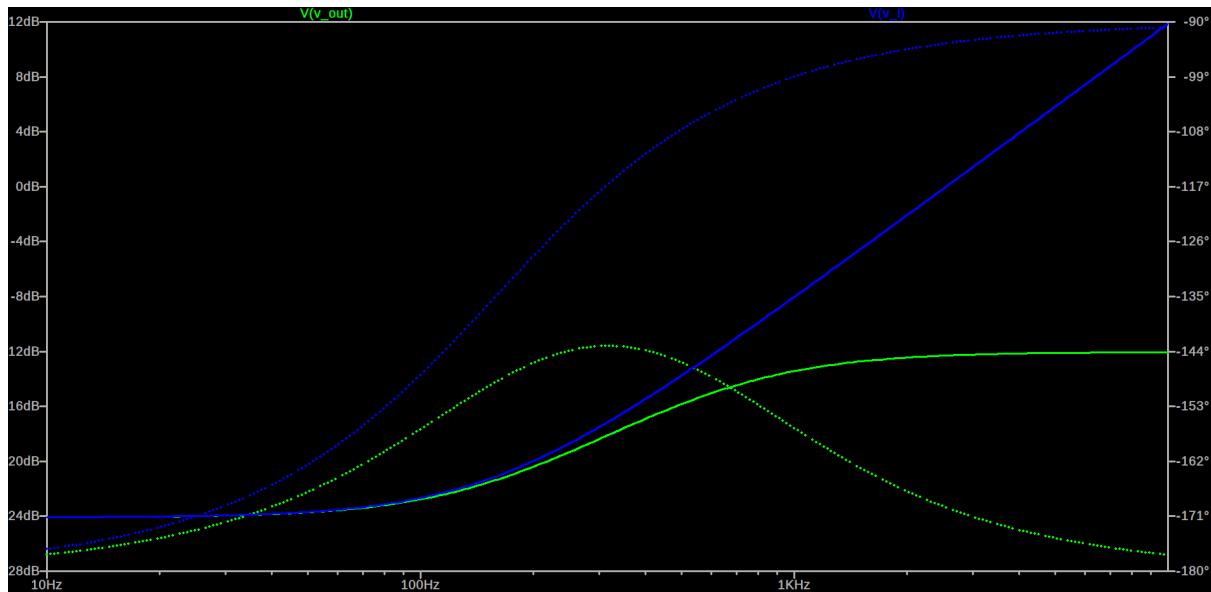
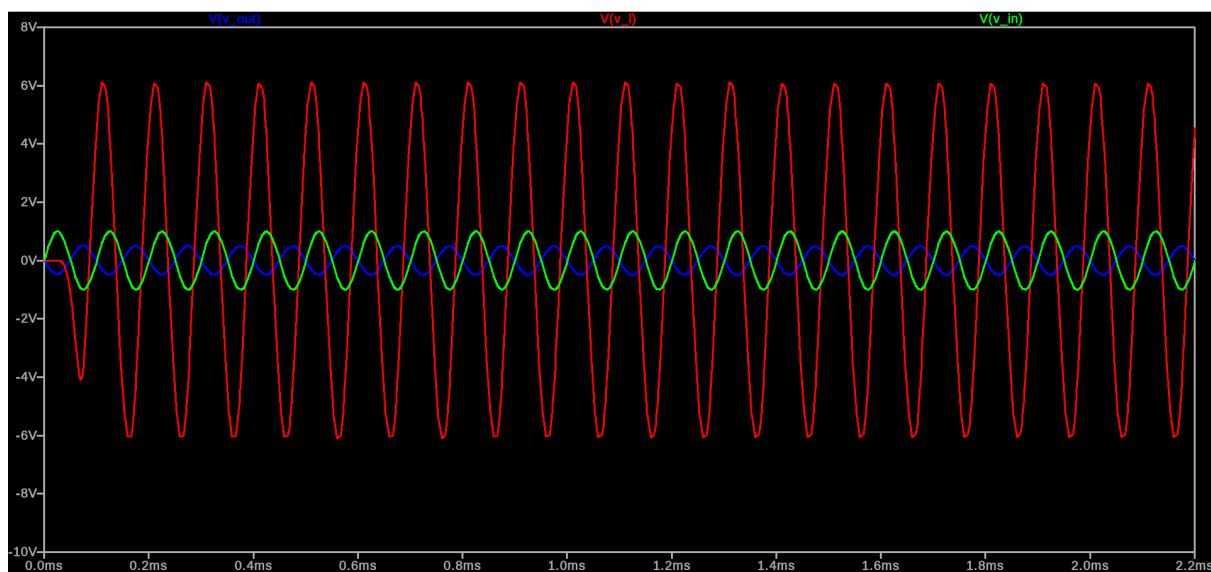
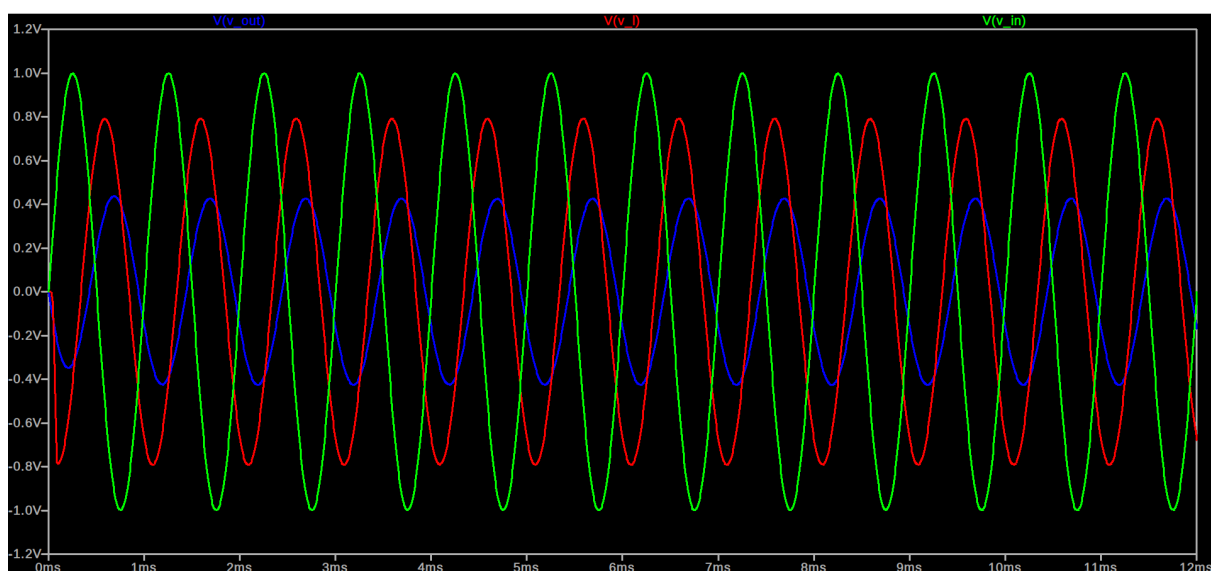


Figure 2.12:  $V_{out}$  &  $H(s)$  Bode Plot

As can be seen in Figure 2.12, output bode plot does not match the transfer function. This is due to pole and zero locations.

- **Pole at  $s = -4000$ :**
  - Pole has negative real part, meaning system is stable. The output will decay over time rather than growing unbounded.
  - The pole at  $s = -4000$  ensures the output responds quickly to changes.
- **Zero at  $s = -1000$ :**
  - Zero has negative real part, meaning it adds a notch or dip in the frequency response.
  - The zero at  $s = -1000$  might suppress or attenuate frequencies associated with noise or other disturbances.
- **Stability:** The system is stable as all poles have negative real part.

Figure 2.13:  $V_{in}$ ,  $V_{out}$  &  $H(s)$  Plot @  $10kHz$ Figure 2.14:  $V_{in}$ ,  $V_{out}$  &  $H(s)$  Plot @  $1kHz$

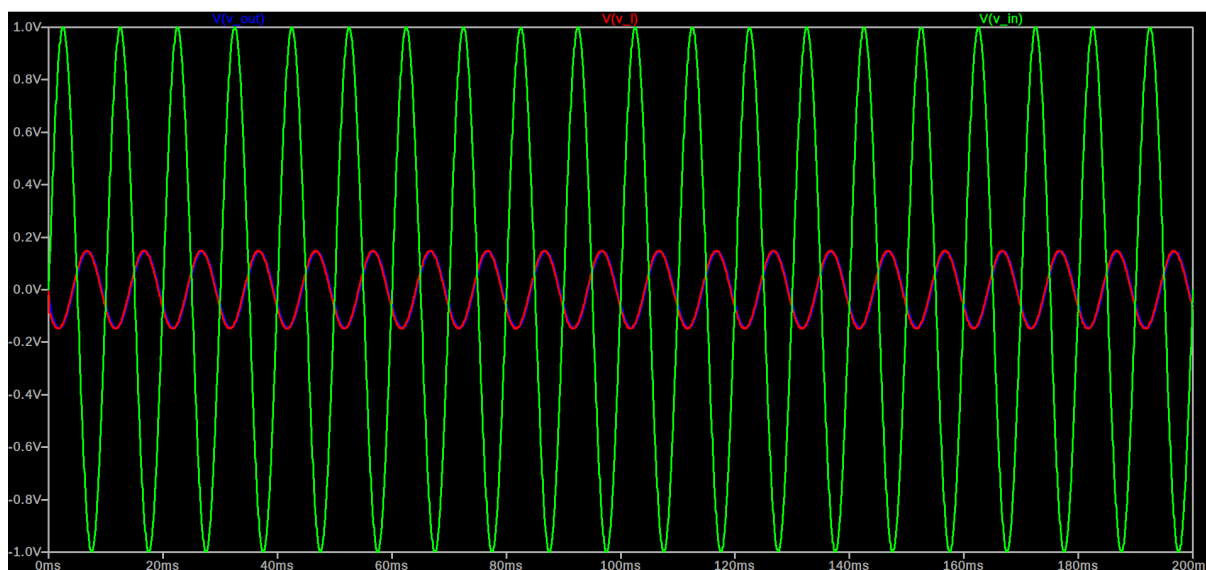


Figure 2.15:  $V_{in}$ ,  $V_{out}$  &  $H(s)$  Plot @  $100Hz$

Plots seen in Figures 2.13, 2.14, and 2.15 show the input and output voltages at  $10kHz$ ,  $1kHz$ , and  $100Hz$  respectively. These graphs confirm the bode plot in Figure 2.12.

# Chapter 3

## Discussion

- **Comparison of Analytical and Simulated Results:** The derived transfer function  $H(s)$  accurately predicted the frequency and transient responses observed in LTSpice simulations.
- **Frequency Response:** The AC Sweep analysis showed that Laplace transform and transfer functions are effective tools for analyzing frequency response that simplifies the process of determining the circuit's behavior at different frequencies.
- **Step Response:** The transient response of the circuit was analyzed using the step response of the circuit. The step response showed that the circuit is stable and has a fast response time.
- **Op-Amp Circuit Behavior:** The op-amp circuit was analyzed using the transfer function  $H(s)$  and the transient response of the circuit. The circuit was found to be stable and had a fast response time. Poles and zeros of the transfer function were used to analyze the stability and characteristics of the circuit and it matched with the results.

# Chapter 4

## Conclusion

This pre-lab demonstrated the effectiveness of the Laplace Transform and LTSpice simulations in analyzing and designing circuits. The step-by-step procedure validated theoretical predictions through simulation. The approach provided valuable insights into frequency and time-domain responses for RLC and op-amp circuits, highlighting the practical application of Laplace Transform in circuit analysis.